
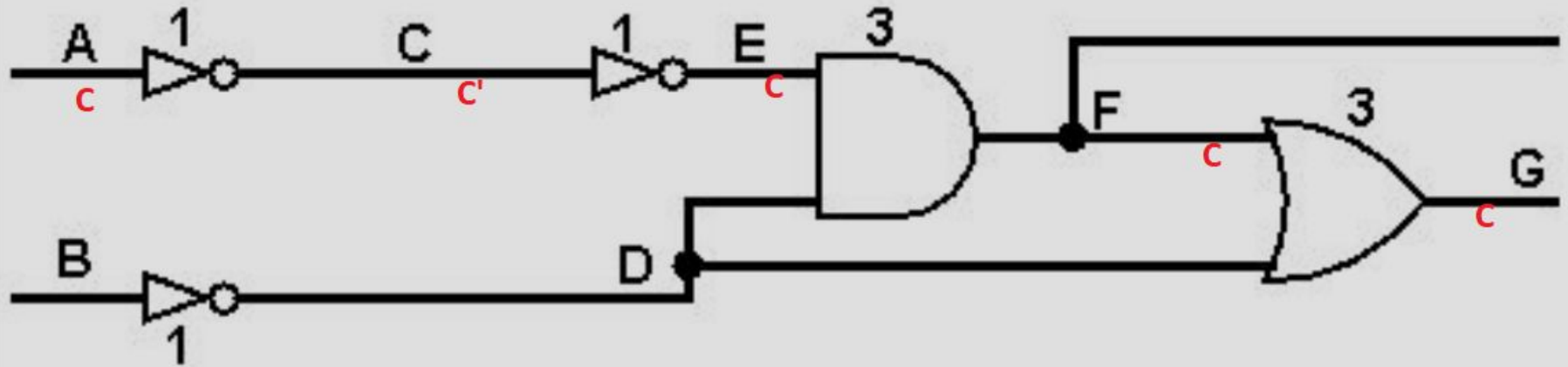



Circuit

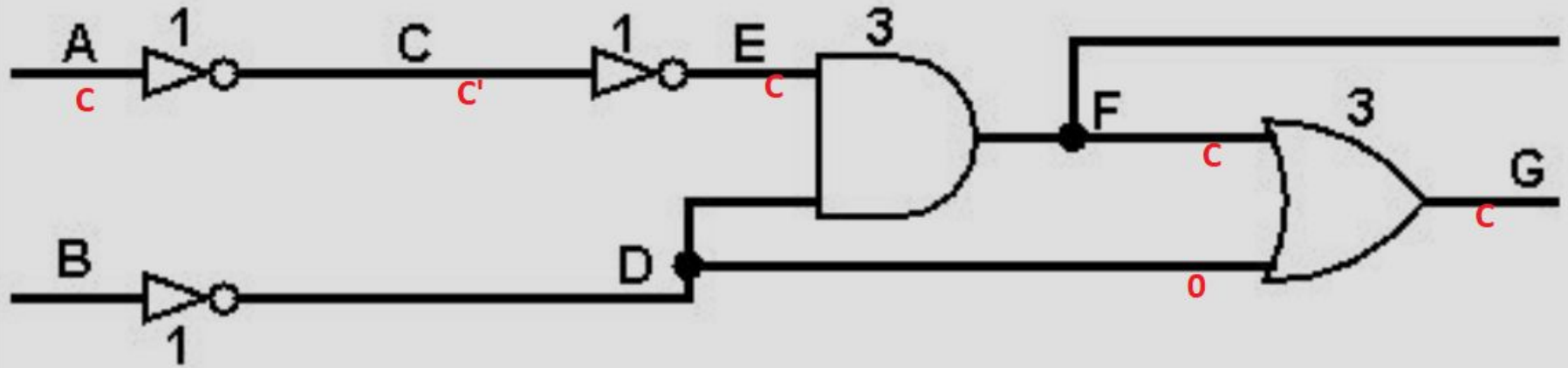


Mark Path A AND2\_1 F OR2\_1 G



Backtrace from PO to PI on path

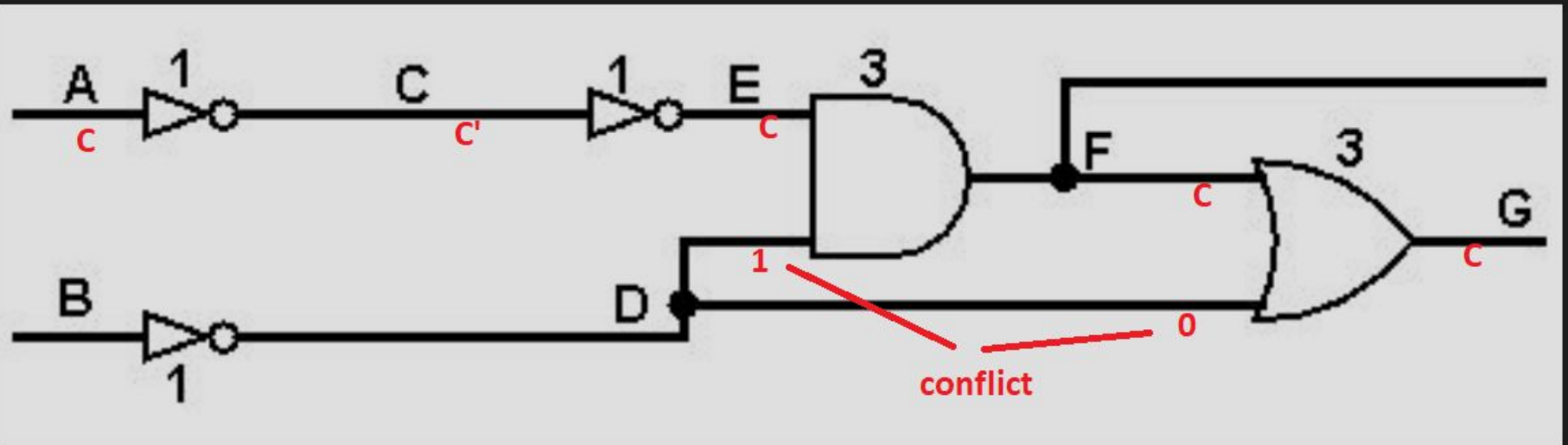

Conflict occurs, backtrack

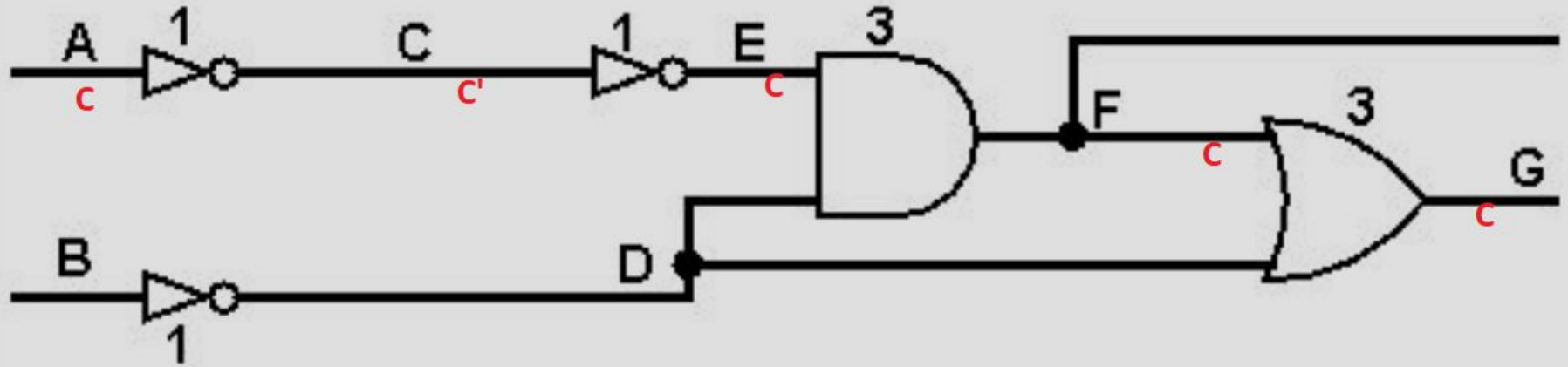

No more untried decisions left - Finish - Path is not sensitizable